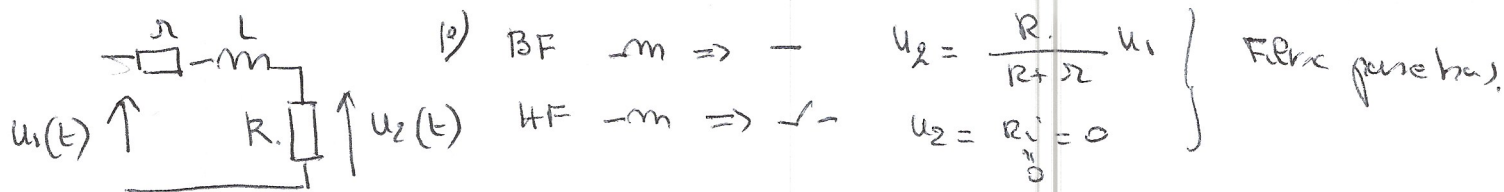


Conecție TD Filtrage



2] $u_1(t) = u_1 \cos \omega t \Rightarrow \underline{u_1} = u_1$
 $u_2(t) = u_2 \cos(\omega t + \varphi) \Rightarrow \underline{u_2} = u_2 e^{j\varphi}$

$H = \frac{u_2}{u_1} = \frac{R}{R + j\omega L} = \frac{R}{R + j\omega L}$

Forma canonică:



$H = \frac{H_0}{1 + j \frac{\omega}{\omega_c}} = |H| e^{j\varphi}$

$H_0 = \frac{R}{R + \omega L} = H(\omega = 0)$

$\omega_c = \frac{R + \omega L}{L} = \text{puterea de câmp}$

BF $\omega < 0,1 \omega_c$ $H \rightarrow H_0$ $G_{dB} \rightarrow Y_{BF} = 20 \log H_0$
 $\varphi \rightarrow 0$

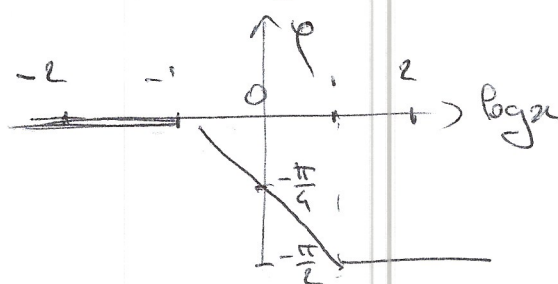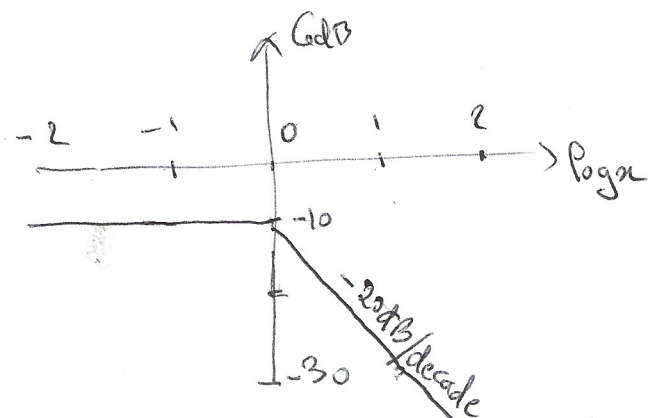HF $\omega > 10 \omega_c$ $H \rightarrow \frac{H_0}{j \frac{\omega}{\omega_c}} \Rightarrow G_{dB} \rightarrow Y_{HF} = 20 \log H_0 - 20 \log \omega$
 $\varphi \rightarrow -\frac{\pi}{2}$



3] $R = 10 \Omega$ $R = 30 \Omega \Rightarrow \frac{R}{R + \omega L} = 0,9 \Rightarrow 20 \log H_0 = 20 \log 0,9$

$f_c = \frac{\omega_c}{2\pi} = \frac{R + \omega L}{L \cdot 2\pi} = \frac{100}{10^2 \cdot 2\pi}$

$f_c = \frac{10^4}{2\pi} = 1592 \text{ Hz}$

* $f_1 = 100 \text{ Hz} \Rightarrow \frac{f}{f_c} = 0,06 \Rightarrow u_s(t) = u_1 \cdot 0,99 \cos(2\pi f_1 t + 0)$

* $f_2 = 10^4 \text{ Hz} \Rightarrow \frac{f}{f_c} = 6,3 \Rightarrow u_s(t) = \frac{u_1 \cdot 0,9}{\sqrt{1 + (6,3)^2}} \cos(2\pi f_2 t - \arctan 6,3)$

$\Rightarrow u_s(t) = 0,14 \cdot u_e \cos(2\pi f_2 t - 1,4)$

4] $T = 0,1 \text{ ms} = 10^{-4} \text{ s} = f_3 = 1 \text{ kHz}$

$u_s(t)$ signal care de frecvență fundamentală $f_0 = 1 \text{ kHz}$

$3f_0 = 3 \text{ kHz}$

$5f_0 = 5 \text{ kHz}$

$\Rightarrow \alpha_0 = \frac{1}{1,6}$

$\alpha_3 = \frac{3}{1,6}$

$\alpha_5 = \frac{5}{1,6}$

①

$$u_s(t) = \frac{4u}{\pi} \left[\frac{0.9}{\sqrt{1 + \left(\frac{1}{1.6}\right)^2}} \cos \left(2\pi f_0 t - \arctan \left(\frac{1}{1.6} \right) \right) \right]$$

$$+ \frac{4u}{3\pi} \left[\frac{0.9}{\sqrt{1 + \left(\frac{3}{1.6}\right)^2}} \cos \left(2\pi (3f_0 t) - \arctan \left(\frac{3}{1.6} \right) \right) \right]$$

$$+ \frac{4u}{5\pi} \left[\frac{0.9}{\sqrt{1 + \left(\frac{5}{1.6}\right)^2}} \cos \left(2\pi (5f_0 t) - \arctan \left(\frac{5}{1.6} \right) \right) \right]$$

$$+ \frac{4u}{7\pi} \left[\frac{0.9}{\sqrt{1 + \left(\frac{7}{1.6}\right)^2}} \cos \left(2\pi (7f_0 t) - \arctan \left(\frac{7}{1.6} \right) \right) \right]$$

Ex2 reception radio.

1) Filtrer porte bande $\rightarrow$ us en serie de R.

$$2) \underline{H} = \frac{\underline{u}_s}{\underline{u}_e} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} = \frac{1}{1 + j(\frac{\omega L}{R} - \frac{1}{R\omega C})}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{L}{R} = \frac{Q}{\omega_0} \Rightarrow$$

$$Q = \frac{1}{R} \cdot \sqrt{\frac{L}{C}}$$

$$\left\{ \begin{aligned} f_0 &= \frac{1}{2\pi\sqrt{LC}} \end{aligned} \right.$$

$$\left\{ \begin{aligned} \text{et } Q = \frac{P_0}{\Delta P} \Rightarrow \Delta P = \frac{P_0}{Q} = \frac{R}{2\pi \cdot L} = \Delta P. \end{aligned} \right. \text{ ne depend pas de } C$$

$$f_1 < f_0 < f_2$$


$$\begin{aligned} f_1 &= 150 \text{ Hz} \\ f_2 &= 300 \text{ Hz} \end{aligned}$$

$$\Rightarrow C_2 < C < C_1$$

$$C_2 = \frac{1}{4\pi^2 f_2^2 \cdot L} = 2,8 \cdot 10^{-10} \text{ F}$$

$$C_1 = \frac{1}{4\pi^2 f_1^2 \cdot L} = 1,1 \cdot 10^{-9} \text{ F}$$

Ex3

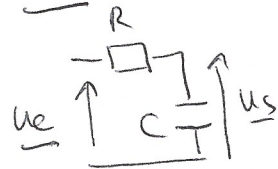

$$\begin{aligned} \underline{H} = \frac{\underline{u}_s}{\underline{u}_e} &= \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC} \\ &= \frac{H_0}{1 + j\frac{\omega}{\omega_0}} \end{aligned}$$


pas de hys l'ordre

$$C \rightarrow \frac{C}{a}$$


$$R \rightarrow aR$$

$$\underline{H} = \frac{\underline{u}_s}{\underline{u}_e} = \frac{\frac{aR}{j\omega C}}{\frac{aR}{j\omega C} + aR} = \frac{1}{1 + j\omega RC}$$

H n'ev pas modifier

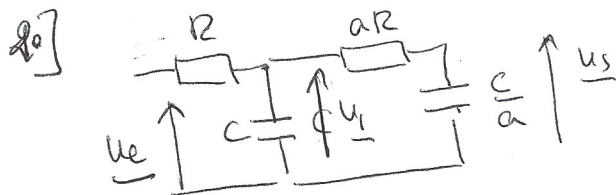
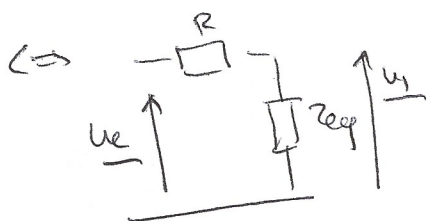
$$\frac{u_s}{u_e} = \frac{u_s}{u_1} \cdot \frac{u_1}{u_e} = \frac{1}{1 + j\omega RC} \cdot \frac{u_1}{u_e}$$



$$\frac{u_1}{u_e} = \frac{Z_{eq}}{R + Z_{eq}} = \frac{1}{1 + R Y_{eq}} = \frac{1}{1 + R \left[j\omega C + \frac{1}{aR + \frac{a}{j\omega C}} \right]}$$

$$\frac{u_i}{u_e} = \frac{1}{1 + jRC\omega + \frac{jRC\omega}{a(1+jRC\omega)}} = \frac{a(1+jRC\omega)}{a[1+jRC\omega]^2 + jRC\omega}$$

$$= \frac{1+jRC\omega}{1 + (2 + \frac{1}{a})jRC\omega + (jRC\omega)^2}$$

$$\Rightarrow \left| \underline{H} = \frac{1}{1 + (2 + \frac{1}{a})jRC\omega + (jRC\omega)^2} = \frac{H_0}{1 + j\frac{\omega}{Q\omega_0} + \left(j\frac{\omega}{\omega_0}\right)^2} \right|$$

Filtre passe bas 2nd ordre.

$$\omega_0 = \frac{1}{RC} \quad RC\left(2 + \frac{1}{a}\right) = \frac{1}{Q\omega_0} \Rightarrow Q = \frac{1}{2 + \frac{1}{a}} < \frac{1}{2} \text{ donc } Q < \frac{1}{\sqrt{2}}$$


pas de résonance

eq. diff. associée :

$$RC^2 \frac{d^2 u_s}{dt^2} + \left(2 + \frac{1}{a}\right) RC \frac{du_s}{dt} + u_s = u_e(t).$$

Si $a \gg 1$ $Q = \frac{1}{2}$ et $\underline{H} = \left(\underline{H}_1\right)^2$ car $Z_e \uparrow \infty$.

Ex 4

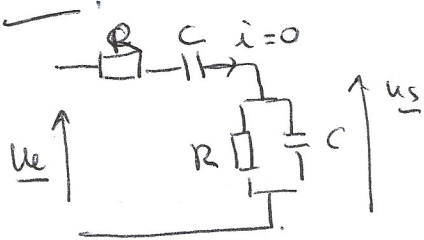

BF $\rightarrow$ $\sqrt{\quad}$

$$u_s = Ri \text{ et } i=0 \rightarrow u_s=0$$

HF $\rightarrow$ ---

$$u_s = 0$$

Passe bande.

$$\frac{u_s}{u_e} = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{1 + Z_1 Y_2} = \frac{1}{1 + \left(R + \frac{1}{j\omega C}\right) \left(\frac{1}{R} + j\omega C\right)}$$

$$= \frac{1}{1 + 1 + jRC\omega + \frac{1}{jRC\omega} + 1} = \frac{1}{3 + j\left(RC\omega - \frac{1}{RC\omega}\right)} = \frac{1/3}{1 + j\left(\frac{RC\omega}{3} - \frac{1}{3RC\omega}\right)}$$

$$= \frac{H_0}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$

$$\Rightarrow H_0 = \frac{1}{3}$$

$$\begin{cases} \frac{RC}{3} = \frac{Q}{\omega_0} \\ \frac{1}{3RC} = \frac{Q \cdot \omega_0}{4} \end{cases}$$

$$\Rightarrow \omega_0 = \frac{1}{RC}$$


$$Q = \frac{1}{3}$$

$$G_{\text{max dB}} = 20 \log H_0 = 20 \log \frac{1}{3} = -9.5 \text{ dB}$$

$$\underline{H} = \frac{H_0}{1+j\varphi(\alpha-\frac{1}{\alpha})} \xrightarrow{\text{BF}} \frac{H_0}{-j\frac{\varphi}{\alpha}} \Rightarrow j\frac{H_0}{\varphi} \cdot \alpha \Rightarrow \begin{cases} G_{\text{dB}} \rightarrow \left| \chi_{\text{BF}} = 20 \log \frac{H_0}{\varphi} + 20 \log \alpha \right. \\ \varphi \rightarrow \frac{\pi}{2} \end{cases}$$

$$\underline{H} = \frac{H_0}{1+j\varphi(\alpha-\frac{1}{\alpha})} \xrightarrow{\text{BF}} \frac{H_0}{j\varphi\alpha} = -j\frac{H_0}{\varphi} \cdot \frac{1}{\alpha} \Rightarrow \begin{cases} G_{\text{dB}} \rightarrow \left| \chi_{\text{HF}} = 20 \log \frac{H_0}{\varphi} - 20 \log \alpha \right. \\ \varphi \rightarrow -\frac{\pi}{2} \end{cases}$$
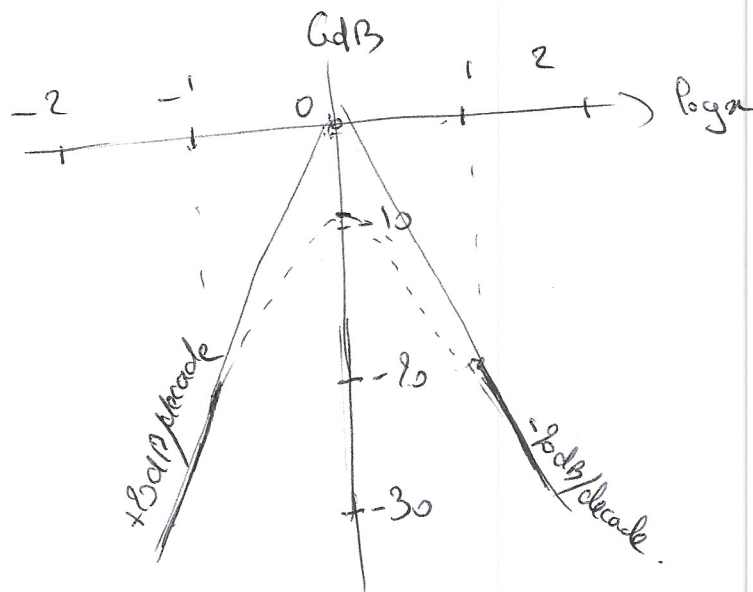
$$\begin{aligned} \text{F} \mid \log \alpha = 0 \quad (\alpha=1) \\ 20 \log \frac{H_0}{\varphi} = 1. \end{aligned}$$



$$50] \omega_0 = \frac{1}{RC} = 2 \cdot 10^3 \text{ rad s}^{-1}.$$

$$\omega_1 = 2 \cdot 10^2 \text{ rad s}^{-1} \Rightarrow \alpha_1 = \frac{\omega_1}{\omega_0} = 0.1$$

$$\omega_2 = 10 \omega_1 = 2 \cdot 10^3 \text{ rad s}^{-1} \quad \alpha_2 = 1.$$

$$\omega_3 = 100 \omega_1 = 2 \cdot 10^4 \text{ rad s}^{-1} \quad \alpha_3 = 10.$$

Rezept $e(t) = \sum E_n \cos(\omega_n t + \varphi_n).$

$$s(t) = \sum E_n \cdot |\underline{H}(\omega_n)| \cos(\omega_n t + \varphi_n + \arg \underline{H}(\omega_n)).$$

$$\arg \underline{H}(\omega) = \arctan \varphi \left(\frac{\omega_n}{\omega} - \frac{\omega}{\omega_n} \right).$$

$$s(t) = \frac{E_0}{10} \cos(\omega_1 t + 1,2) + \frac{E_0}{3} \cos(10\omega_1 t) + \frac{E_0}{10} \cos(100\omega_1 t + 1,2)$$

les lecture des diagrammes de Bode.

$$e(t) = \sum_n E_n \cos(\omega_n t + \varphi_n)$$

$$s(t) = \sum |H(\omega_n)| \cdot E_n \cos(\omega_n t + \varphi_n + \arg H(\omega_n))$$

$$\omega \quad |H(\omega_n)| = 10^{GdB(\omega_n)/20} \quad \text{et}$$

1^o filtre passe haut $f_0 = 10 \text{ kHz}$ sur resonance.

$$f_1 = 1 \text{ kHz} \Rightarrow \alpha_1 = \frac{f_1}{f_0} = 0,1$$

$$e_1(t) \quad \text{frequence } f_1 \rightarrow \alpha_1 = 0,1$$

$$e_2(t) \quad 10f_1 = f_2 \rightarrow \alpha_2 = 1$$

$$e_3(t) \quad 100f_1 = f_3 \rightarrow \alpha_3 = 10$$

$$e(t) = e_0 + e_1(t) + e_2(t) + e_3(t)$$

$$s(t) = s_0 + s_1(t) + s_2(t) + s_3(t)$$

$$s_0 = 0$$

$s_1 \neq 0$ car atténuation de 40 dB $\Rightarrow$ division de l'amplitude par 100.

$$s_2(t) = E_0 \cdot \underbrace{10^{-GdB/20}}_{\substack{10^{-\frac{1}{2}} \\ \approx 0,3}} \cos\left(f_2 t + \frac{\pi}{4} + \frac{\pi}{2}\right) = 0,3 E_0 \cos\left(f_2 t + \frac{3\pi}{4}\right)$$

$$s_3(t) \approx e_3(t) =$$

2^o filtre passe haut resonant. $f_1 = 100 \text{ kHz}$.

Caractéristique coupée $\rightarrow s(t) = e(t) - e_0$

3^o filtre. rejection $f_0 = 1 \text{ kHz}$.

$$s(t) = e(t) - e_1(t)$$

1° P. 1ère pour les 1° ordre. $f_0 = 100 \text{ Hz}$. $H_0 = 1$.

$$s_0 = e_0.$$

$e_1(t)$ de fréquence $10 f_0$. Amplitude de $s_1(t)$ divisée par 10.
 $\varphi_H = -\frac{\pi}{2}$.

$e_2(t)$ de fréquence $100 f_0$ Amplitude de $s_2(t)$ divisée par 100, $\varphi_H = -\frac{\pi}{2}$
 $e_3(t)$ " " $1000 f_0$ " " " " " "

$$s(t) = E_0 + \frac{E_0}{10} \cos\left(\omega t - \frac{\pi}{2}\right) + \frac{E_0}{100} \cos\left(10\omega t - \frac{\pi}{2}\right) + \frac{E_0}{1000} \cos\left(100\omega t - \frac{5\pi}{6}\right).$$